

## EE 252: Electrical Machines and Power Electronics Lab (EMPEL) DC-DC Converter Project



Set Number (E): 1

Batch Number (B): 9

Roll. Nos of students: 230002008, 230002019, 230002031, 230002038

### Problem Statement :

*Buck - Boost Converter*

- Specifications: Input 20 V, Output 15-25 V, Switching frequency 10 kHz, Output current 1 A. Waveforms of diode current and switch voltage in CCM.
- Reduce switching frequency to demonstrate DCM.

### Observations

For an input of 20V we observed output of


DCM Mode is observed at 3.203kHz when decreased switching frequency from 10kHz.

Output Voltage for 20V input at 10kHz frequency:


- Buck (at 42.8% Duty Cycle) = 15V
- Boost (at 55.5% Duty Cycle) = 25V

$$I_{Lavg} = I_g + I_o = 0.99A + 1.28A = 2.27A$$

### Snapshots of Hardware Implementation

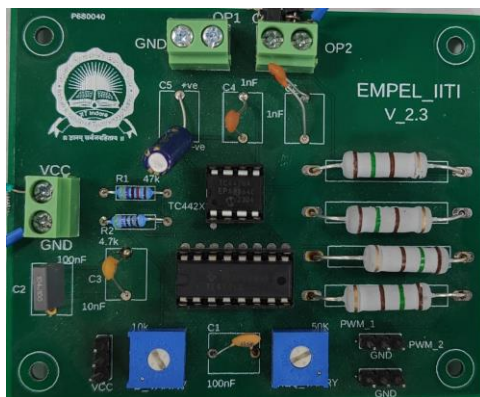


PWM Generator (TL494 IC) PCB

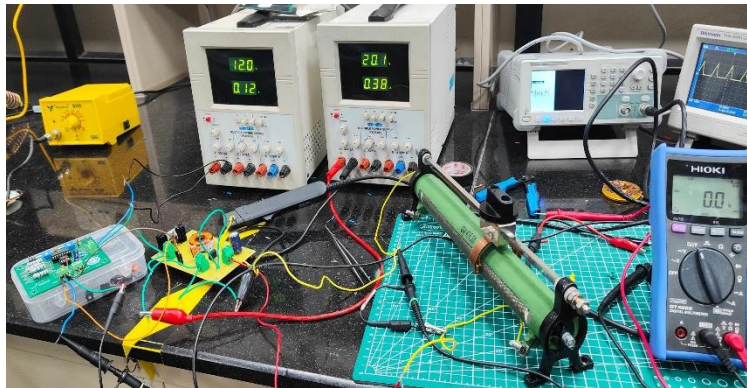


BUCK-BOOST Converter Circuit Set-up

**PWM Waveform:**

Duty Cycle 27.9%:

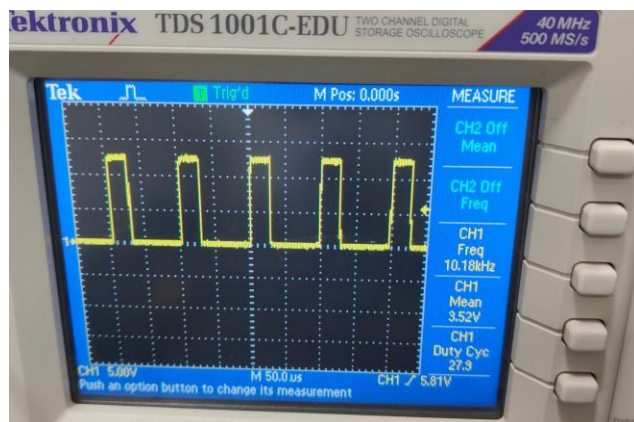


Duty Cycle 60.3%:

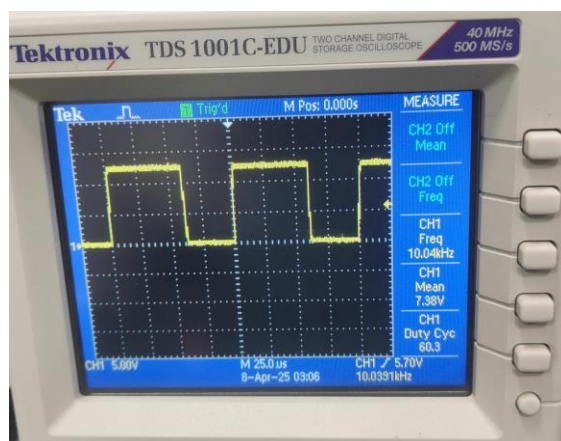


### Inductor Current Waveform:


Continuous Conduction Mode (CCM):

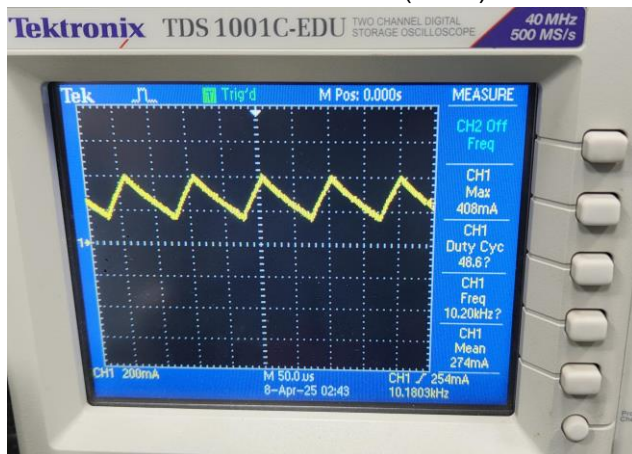

Boundary Conduction Mode (BCM):

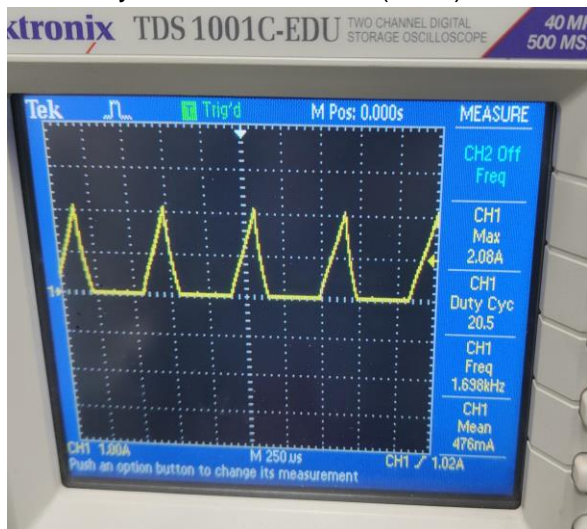

Discontinuous Conduction Mode (DCM):

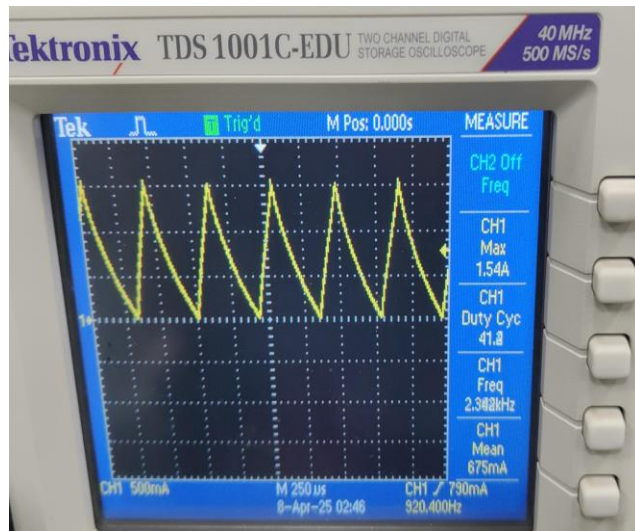

Diode Current Waveform:

